

Semester Project Proposal

Subject : DLD LAB

Project Title : Password Security System

Group Members:

<u>Names</u>	<u>Reg No</u>
Mahad Khan	23MDBCS-341
Muhammad Talha	23MDBCS-347
Rifaq Ajmal	23MDBCS-435
Rohail Muneer	23MDBCS-450

Introduction To The Project

Creating a Digital Logic Design (DLD) project on a password security system involves designing a circuit that checks if a user-entered password matches a predefined password. Here's a simple outline of such a project:

Components Needed:

1. Logic Gates (AND, OR, NOT)
2. Flip-Flops (D Flip-Flops for memory)
3. Input Switches (for entering the password)
4. LEDs (to indicate success or failure)

Circuit Description:

1. Use D Flip-Flops to store the password. Each flip-flop represents a bit of the password.
2. Use a series of logic gates (AND, OR, NOT) to compare the user-entered password with the stored password.
3. Use input switches to enter the password.
4. Use LEDs to indicate whether the entered password is correct or not.

Detailed Steps:

1. Design a D Flip-Flop based memory unit to store the password.
2. Design a circuit to compare the user-entered password with the stored password.
3. Use logic gates to check if each bit of the user-entered password matches the corresponding bit of the stored password.
4. Use LEDs to indicate whether the entered password is correct or not.
5. Test the circuit with different passwords to ensure its functionality.

Note:

- This is a basic outline, and you can add more features like multiple user support, password change functionality, etc., based on your project requirements.
 - Implementing this project requires a good understanding of digital logic design and the ability to work with logic gates and flip-flops.
-