



UNIVERSITY OF ENGINEERING AND TECHNOLOGY MARDAN

NAME	RIFAQ AJMAL
REG NO	23MDBCS435
SECTION	A
DEPPT	COMPUTER SCIENCE
SUBJECT	DLD LAB
TEACHER	SHAHZAD SIR

LAB TASK : 9

Adder-Subtractor


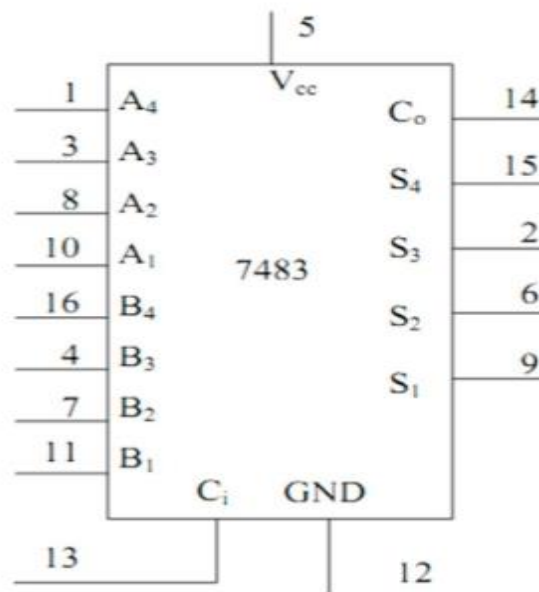


Figure 9.1: IC type 7483 4-bit adder

Circuit Diagram:

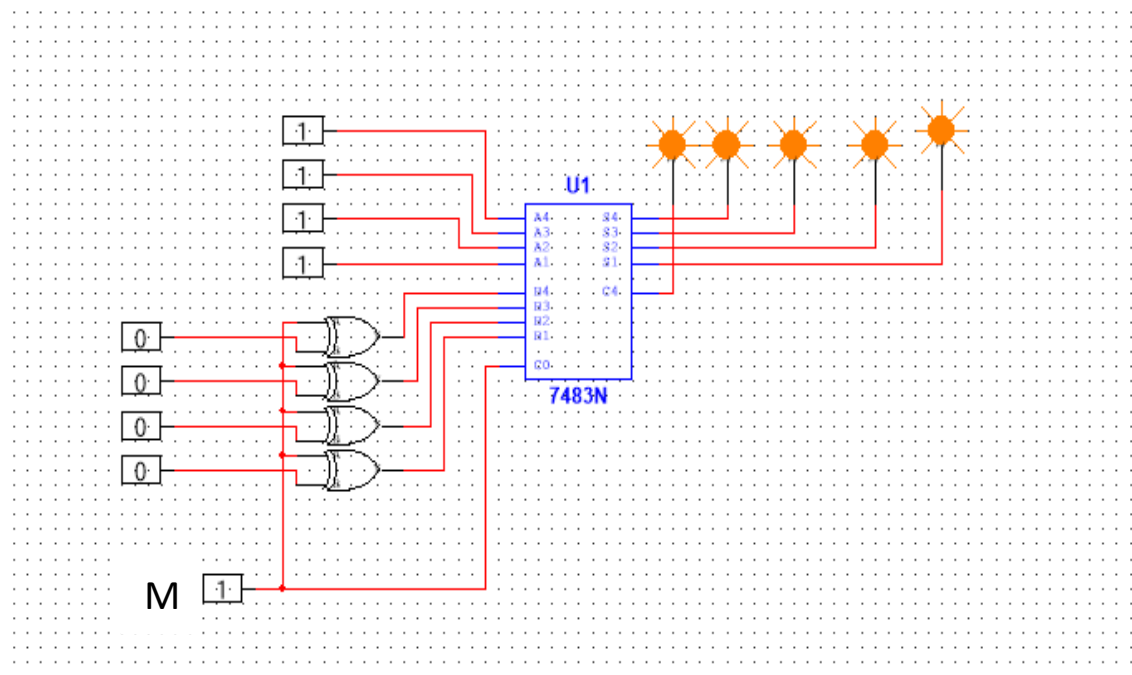

M=0 to add two 4bit binary numbers

M=0 is to subtract one from the other

TABLE FOR SUM:

A3	A2	A1	A0	B3	B2	B1	B0	SUM				C
1	0	0	1	0	0	1	0	1	0	1	1	0
0	1	1	0	1	0	1	1	0	0	0	1	1
1	1	0	0	1	0	1	0	0	1	1	0	1

TABLE FOR Subtraction:

	A3	A2	A1	A0	B3	B2	B1	B0	SUB				B
A>B	1	0	0	1	0	0	1	0	0	1	1	1	1
A<B	0	1	1	0	1	0	1	1	1	0	1	1	0
A>B	1	1	0	0	1	0	1	0	0	0	1	0	1

THE END